

**ECE 198JL Third Midterm Exam
Spring 2013**

Tuesday, April 9th, 2013

Name: _____	NetID: _____	
Discussion Section:		
10:00 AM	<input type="checkbox"/> JD1	
11:00 AM	<input type="checkbox"/> JD2	
2:00 PM	<input type="checkbox"/> JD3	
4:00 PM	<input type="checkbox"/> JD4	


-
- **Be sure your exam booklet has 11 pages.**
 - **Be sure to write your name and lab section on the first page.**
 - **Do not tear the exam booklet apart; you can only detach the last page.**
 - **We have provided LC-3 instructions set at the back.**
 - **Use backs of pages for scratch work if needed.**
 - **This is a closed book exam. You may not use a calculator.**
 - **You are allowed one handwritten 8.5 x 11" sheet of notes.**
 - **Absolutely no interaction between students is allowed.**
 - **Be sure to clearly indicate any assumptions that you make.**
 - **The questions are not weighted equally. Budget your time accordingly.**
 - **Don't panic, and good luck!**
-

Problem 1	8 points:	_____
Problem 2	6 points:	_____
Problem 3	16 points:	_____
Problem 4	11 points:	_____
Problem 5	12 points:	_____
Problem 6	23 points:	_____
Problem 7	9 points:	_____
Problem 8	15 points:	_____

Total	100 points:	_____
-------	-------------	-------

 Problem 1 (8 pts): Sequential circuit analysis

Consider the Finite State Machine (FSM) shown below that has three internal state bits, $Q_2Q_1Q_0$, and three outputs, $Z_2Z_1Z_0$, that match the internal state bits, that is, $Z_i = Q_i$.



1. Write Boolean expressions for the flip-flop inputs D_2 , D_1 and D_0 (flip-flop excitation equations) as functions of current state $Q_2Q_1Q_0$:

$D_2 =$ _____

$D_1 =$ _____

$D_0 =$ _____

2. Fill in the next-state table and output table


Current state			Next state		
Q_2	Q_1	Q_0	Q_2^+	Q_1^+	Q_0^+
0	0	0			
0	0	1			
0	1	0			
0	1	1			
1	0	0			
1	0	1			
1	1	0			
1	1	1			

3. Draw the state transition diagram for this FSM.

4. Explain the function of this FSM.

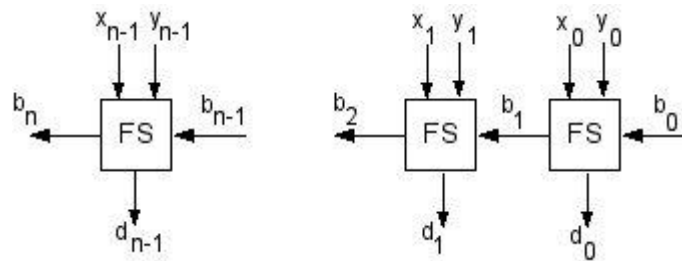Problem 2 (6 pts): Serial design


In Midterm 2 you designed a bit-sliced *ripple borrow* subtractor circuit consisting of n Full Subtractor (FS) bit slice cells:



1. How many flip-flops are needed to construct a *serial* subtractor circuit using a Mealy machine model?

Answer: _____

 
2. Re-draw the bit-sliced design shown above as a serial design using a Mealy machine model



3. How many flip-flops are needed to construct a *serial* subtractor circuit using a Moore machine model?


Answer: _____

 4. Re-draw the bit-sliced design shown above as a serial design using a Moore machine model



 Problem 3 (16 pts): RAM


Shown to the right is a 1M x 24 RAM. ($1M = 2^{20}$.)



1. How many bits **addr**, **data**, **CS**, and **r/w'** ports require?

Answer: addr: _____ CS: _____
 data: _____ r/w': _____

 2. Implement this RAM using 16Kx8 RAM chips. Each 16Kx8 RAM chip has inputs **data**, **addr**, **CS**, and **r/w'**, and output gated by a tri-state buffer. Finish the implementation by drawing the missing connections and labeling all newly added wires. (You do not need to draw all the rows, they are shown as " ... ", but be sure the pattern is clear.) The RAM output wires and CS are already drawn for you.



3. How many rows of 16Kx8 RAM chips are needed and what is the value of k ?

Number of rows: _____ $k =$ _____?

4. Suppose you wish to store the decimal value -4 in memory at the address 16,416. In which 16Kx8 RAM chip(s) will this value be stored?


Answer: _____

5. What input values must be provided to the corresponding 16Kx8 RAM chip(s) in order to properly store this value? Give the **addr** and **data** values for *each chip* in hexadecimal.

addr: _____ data: _____

 Problem 4 (11 pts): Counter design

Using conventional sequential circuit design technique, implement a 3-bit synchronous counter with D flip-flops that counts in the following $Q_2Q_1Q_0$ sequence:



1. Show K-maps for D_2 , D_1 , D_0 :

		Q_1Q_0			
		0	0	1	1
		0		1	0
Q	0				
	1				
D_2					

		Q_1Q_0			
		0	0	1	1
		0		1	0
Q	0				
	1				
D_1					

		Q_1Q_0			
		0	0	1	1
		0		1	0
Q	0				
	1				
D_0					


2. Write Boolean expressions for D_2 , D_1 , D_0 :

$D_2 =$ _____

$D_1 =$ _____

$D_0 =$ _____

 3. Draw the circuit using only 2 additional gates.



4. Is your counter *self-starting*? Explain - and be specific to *your solution*. (Self-starting means that no matter in what state the counter starts, it always converges to produce the correct counting sequence.)

Problem 5 (12 pts): Sequence recognizer design

Design a sequence recognizing FSM with input x and output z such that the output is 1 if and only if pattern **01** or **110** has been detected in the input stream. Make sure to detect overlapping patterns.

Example:

Input:	0	0	1	0	1	0	1	1	0	1	1	0	1	0	1	1	0	1	0...
Output:	0	0	1	0	1	0	1	0	1	1	0	1	1	0	1	0	1	1	0...

1. Draw the Moore state diagram, using as few states as possible. (Solutions with more than 6 states are not acceptable.) Let A be the start state. Each edge must be labeled with x and each node must be labeled with *name/z*.

2. Write down *state meaning* and choose their binary *representations* $S_2S_1S_0$:

Problem 6 (23 pts): Two-floor elevator controller FSM

You are tasked with designing a two-floor elevator electronic control system. The elevator moves between just two floors, floor #1 and floor #2. It is controlled by 2 buttons: UP and DOWN. When a user presses button UP, input signal U becomes 1, otherwise it is 0. When user presses button DOWN, input signal D becomes 1, otherwise it is 0. The control unit generates output signals G_u (go up) and G_d (go down) to control the electric motor that moves the elevator one floor up (when $G_u=1$) or down (when $G_d=1$). When user presses both buttons at the same time, the elevator should not move.

1. Design a Moore state machine implementing this system. Determine the states you need, giving them meaningful names so that we can comprehend your design intent, and sketch the complete state transition diagram for your FSM, specifying inputs U and D for each transition and outputs G_u and G_d for each state. (*You do not need more than 4 states.*)
2. Fill in the truth table below by assigning internal state bit representations S_1S_0 and output values G_d and G_u for each of your states from Part 1 and then filling in the values for the next-state variables S_1^+ and S_0^+ for each combination of S_1S_0UD .

State name and meaning	Current state		External Inputs		Next state		External outputs	
	S_1	S_0	U	D	S_1^+	S_0^+	G_u	G_d
			0	0				
			0	1				
			1	0				
			1	1				
			0	0				
			0	1				
			1	0				
			1	1				
			0	0				
			0	1				
			1	0				
			1	1				
			0	0				
			0	1				
			1	0				
			1	1				

3. Using the truth table that you wrote in Part 2, fill in the K-maps for S_1^+ , S_0^+ , G_d , and G_u and derive Boolean expressions for these variables.

		S_1	
		0	1
S_0	0		
	1		

		S_1	
		0	1
S_0	0		
	1		

$G_u =$ _____

$G_d =$ _____


		$S_1 S_0$			
		00	01	11	10
UD	00				
	01				
	11				
	10				

		$S_1 S_0$			
		00	01	11	10
UD	00				
	01				
	11				
	10				

$S_1^+ =$ _____

$S_0^+ =$ _____

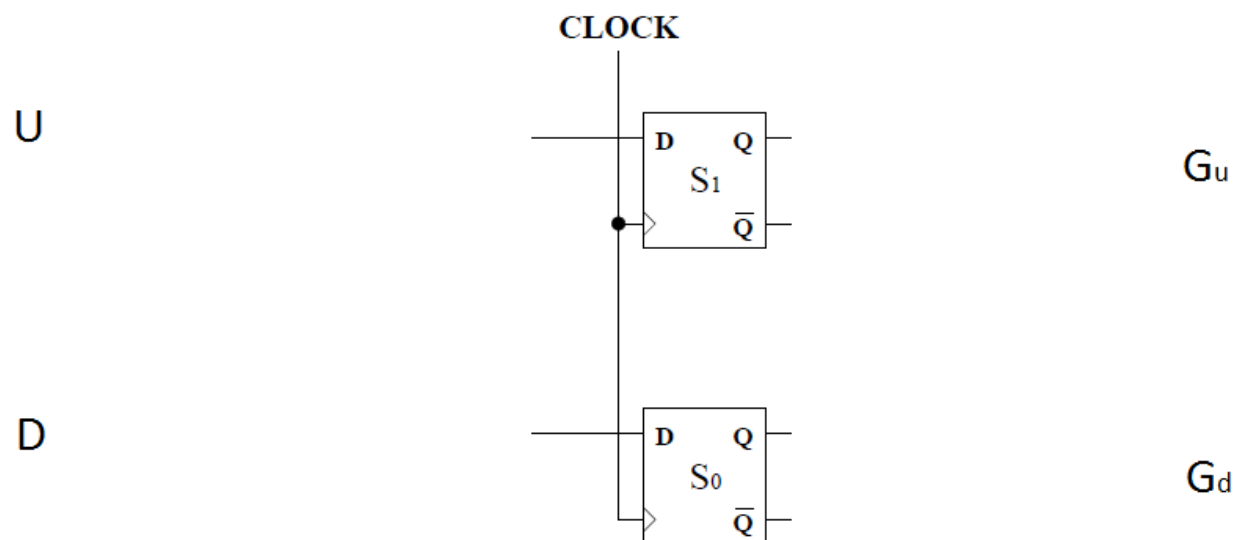4. Add gates as necessary to complete the implementation of your FSM using the two positive edge-triggered D flip-flops shown below.



Problem 7 (9 pts): Von Neumann architecture

1. Name all components of the von Neumann architecture and briefly describe their function.

2. List all phases of the von Neumann instruction cycle.

3. Describe the purpose of the following registers in the von Neumann architecture.

PC:

IR:

MDR:

MAR:

General-purpose register file:

Problem 8 (15 pts): LC-3 ISA

The following LC-3 program fragment, represented as three hexadecimal numbers, is stored in memory at the indicated locations and the following values are stored in registers:

address	instruction
...	
x4001	x6081
x4002	x1204
x4003	x0110
...	

register	value
R0	x4000
R1	x4001
R2	x4002
R3	x4003
R4	x4004

1. Re-write first two instructions in binary representation and provide their corresponding RTL. (Note: formats of the entire LC-3 instruction set are provided at the end of the exam booklet.)

address	instruction	binary instruction	RTL (be specific to this instruction)
...			
x4001	x6081		
x4002	x1204		
...			

2. Assuming PC is initially set to x4001, trace the execution of **two** steps of the given program segment and fill in the table below. Write down values stored in PC, IR, MAR, MDR, N, Z, and P registers **at the end of the instruction cycle**. Values for PC, IR, MAR, and MDR should be written in hexadecimal. Values for N, Z, and P, if known, should be written in binary, or marked with X if they cannot be determined based on the provided information.

PC	IR	MAR	MDR	N	Z	P

3. What hexadecimal value will be stored in R1 once the two instructions are executed?

Answer: _____

4. What is the address of the next instruction to be executed after executing these two instructions?

Answer: _____

5. How many memory reads will take place in order to execute these two instructions, including instruction FETCH?

6. Answer: _____

NOTES: RTL corresponds to execution (after fetch!); JSRR not shown

ADD	<table><tr><td>0001</td><td>DR</td><td>SR1</td><td>0</td><td>00</td><td>SR2</td></tr></table>	0001	DR	SR1	0	00	SR2	ADD DR, SR1, SR2	LD	<table><tr><td>0010</td><td>DR</td><td></td><td></td><td></td><td>PCoffset9</td></tr></table>	0010	DR				PCoffset9	LD DR, PCoffset9
0001	DR	SR1	0	00	SR2												
0010	DR				PCoffset9												
	DR ← SR1 + SR2, Setcc			DR ← M[PC + SEXT(PCoffset9)], Setcc													
ADD	<table><tr><td>0001</td><td>DR</td><td>SR1</td><td>1</td><td></td><td>imm5</td></tr></table>	0001	DR	SR1	1		imm5	ADD DR, SR1, imm5	LDI	<table><tr><td>1010</td><td>DR</td><td></td><td></td><td></td><td>PCoffset9</td></tr></table>	1010	DR				PCoffset9	LDI DR, PCoffset9
0001	DR	SR1	1		imm5												
1010	DR				PCoffset9												
	DR ← SR1 + SEXT(imm5), Setcc			DR ← M[MPC + SEXT(PCoffset9)], Setcc													
AND	<table><tr><td>0101</td><td>DR</td><td>SR1</td><td>0</td><td>00</td><td>SR2</td></tr></table>	0101	DR	SR1	0	00	SR2	AND DR, SR1, SR2	LDR	<table><tr><td>0110</td><td>DR</td><td>BaseR</td><td></td><td></td><td>offset6</td></tr></table>	0110	DR	BaseR			offset6	LDR DR, BaseR, offset6
0101	DR	SR1	0	00	SR2												
0110	DR	BaseR			offset6												
	DR ← SR1 AND SR2, Setcc			DR ← M[BaseR + SEXT(offset6)], Setcc													
AND	<table><tr><td>0101</td><td>DR</td><td>SR1</td><td>1</td><td></td><td>imm5</td></tr></table>	0101	DR	SR1	1		imm5	AND DR, SR1, imm5	LEA	<table><tr><td>1110</td><td>DR</td><td></td><td></td><td></td><td>PCoffset9</td></tr></table>	1110	DR				PCoffset9	LEA DR, PCoffset9
0101	DR	SR1	1		imm5												
1110	DR				PCoffset9												
	DR ← SR1 AND SEXT(imm5), Setcc			DR ← PC + SEXT(PCoffset9), Setcc													
BR	<table><tr><td>0000</td><td>n</td><td>z</td><td>p</td><td></td><td>PCoffset9</td></tr></table>	0000	n	z	p		PCoffset9	BR[nzp] PCoffset9	NOT	<table><tr><td>1001</td><td>DR</td><td>SR</td><td></td><td></td><td>1111111</td></tr></table>	1001	DR	SR			1111111	NOT DR, SR
0000	n	z	p		PCoffset9												
1001	DR	SR			1111111												
	((n AND N) OR (z AND Z) OR (p AND P)): PC ← PC + SEXT(PCoffset9)			DR ← NOT SR, Setcc													
JMP	<table><tr><td>1100</td><td>000</td><td>BaseR</td><td></td><td></td><td>000000</td></tr></table>	1100	000	BaseR			000000	JMP BaseR	ST	<table><tr><td>0011</td><td>SR</td><td></td><td></td><td></td><td>PCoffset9</td></tr></table>	0011	SR				PCoffset9	ST SR, PCoffset9
1100	000	BaseR			000000												
0011	SR				PCoffset9												
	PC ← BaseR			M[PC + SEXT(PCoffset9)] ← SR													
JSR	<table><tr><td>0100</td><td>1</td><td></td><td></td><td></td><td>PCoffset11</td></tr></table>	0100	1				PCoffset11	JSR PCoffset11	STI	<table><tr><td>1011</td><td>SR</td><td></td><td></td><td></td><td>PCoffset9</td></tr></table>	1011	SR				PCoffset9	STI SR, PCoffset9
0100	1				PCoffset11												
1011	SR				PCoffset9												
	R7 ← PC, PC ← PC + SEXT(PCoffset11)			M[MPC + SEXT(PCoffset9)] ← SR													
TRAP	<table><tr><td>1111</td><td>0000</td><td></td><td></td><td></td><td>trapvect8</td></tr></table>	1111	0000				trapvect8	TRAP trapvect8	STR	<table><tr><td>0111</td><td>SR</td><td>BaseR</td><td></td><td></td><td>offset6</td></tr></table>	0111	SR	BaseR			offset6	STR SR, BaseR, offset6
1111	0000				trapvect8												
0111	SR	BaseR			offset6												
	R7 ← PC, PC ← M[ZEXT(trapvect8)]			M[BaseR + SEXT(offset6)] ← SR													