

## ECE 198JL Second Midterm Exam Spring 2014

Tuesday, March 11<sup>th</sup>, 2014

Name: \_\_\_\_\_ NetID: \_\_\_\_\_

Discussion Section:

9:00 AM	<input type="checkbox"/>	JD9	<input type="checkbox"/>	JDA
10:00 AM	<input type="checkbox"/>	JD1		
11:00 AM	<input type="checkbox"/>	JD2	<input type="checkbox"/>	JDB
12:00 PM	<input type="checkbox"/>	JD5		
1:00 PM	<input type="checkbox"/>	JD6	<input type="checkbox"/>	JD7
2:00 PM	<input type="checkbox"/>	JD3		
3:00 PM	<input type="checkbox"/>	JD8		
4:00 PM	<input type="checkbox"/>	JD4	<input type="checkbox"/>	JDC

- **Be sure your exam booklet has 13 pages.**
- **Be sure to write your name and lab section on the first page.**
- **Do not tear the exam booklet apart; you can only detach the last page.**
- **We have provided Boolean properties at the back.**
- **Use backs of pages for scratch work if needed.**
- **This is a closed book exam. You may not use a calculator.**
- **You are allowed one handwritten 8.5 x 11" sheet of notes.**
- **Absolutely no interaction between students is allowed.**
- **Be sure to clearly indicate any assumptions that you make.**
- **The questions are not weighted equally. Budget your time accordingly.**
- **Don't panic, and good luck!**

Problem 1	12 points:	_____
Problem 2	12 points:	_____
Problem 3	11 points:	_____
Problem 4	9 points:	_____
Problem 5	17 points:	_____
Problem 6	17 points:	_____
Problem 7	12 points:	_____
Problem 8	10 points:	_____

---

Total	100 points:	_____
-------	-------------	-------

**Problem 1 (12 pts): Boolean algebra**

1. (5 pts) Which Boolean expressions below are equivalent to the Boolean expression  $f(a, b, c, d) = \overline{a}c + bc + a\bar{c}$ ? [More than one answer may be equivalent]

a)  $f(a, b, c, d) = \overline{a}c + ab + a\bar{c}$

b)  $f(a, b, c, d) = \overline{c(b + \bar{a}) + a\bar{c}}$

c)  $f(a, b, c, d) = (\bar{a} + c)(a + \bar{c})(\bar{b} + \bar{c})$

d)  $f(a, b, c, d) = (b + c)(\bar{a} + c)(a + \bar{c})$

e)  $f(a, b, c, d) = a\bar{c} + \bar{a}c + bc$

2. (5 pts) Which Boolean expressions below are equivalent to the Boolean expression  $f(a, b, c) = a + bc + \bar{c}$ ? [More than one answer may be equivalent]

a)  $f(a, b, c) = (a + b)(a + c) + \bar{c}$

b)  $f(a, b, c) = a + \bar{c}$

c)  $f(a, b, c) = (a + b)a + \bar{c}$

d)  $f(a, b, c) = (a + b + \bar{c})(a + c)$

e)  $f(a, b, c) = a + b + \bar{c}$

3. (2 pts) The function  $f(w, x, y, z) = m_3 \cdot m_4$ , where  $m_3$  and  $m_4$  are minterms. Which expression below is equivalent to  $f(w, x, y, z)$ ?

a)  $m_7$

b)  $M_8$

c)  $M_3 + M_4$

d) 0

e) 1

**Problem 2 (12 pts): Karnaugh Maps**

Consider a 4-variable Boolean function  $f(w, x, y, z)$  given by its K-map (drawn twice):


		yz			
		00	01	11	10
wx	00	0	1	1	1
	01	1	1	0	0
	11	1	1	0	1
	10	0	0	1	1

		yz			
		00	01	11	10
wx	00	0	1	1	1
	01	1	1	0	0
	11	1	1	0	1
	10	0	0	1	1

- (2pts)** How many prime implicants are in the K-map?  
 a) 4                      b) 5                      **c) 6**                      d) 7                      e) 8 or more
- (2pts)** How many essential prime implicants are in the K-map?  
 a) 0                      b) 1                      **c) 2**                      d) 3                      e) 4
- (2pts)** The k-map has how many minimal SOP Boolean expressions?  
 a) 1                      b) 2                      c) 3                      **d) 4**                      e) 5
- (2pts)** The minimal SOP Boolean expression has how many product terms?  
 a) 1                      b) 2                      c) 3                      **d) 4**                      e) 5
- (2pts)** The minimal SOP Boolean expression has how many literals (include duplicates in your count:  $x'y + x'z$  would count as four literals)?  
 a) 7                      **b) 10**                      c) 13                      d) 14                      e) 16  
3 + 3 + 2 + 2
- (2pts)** The minimal POS and minimal SOP expressions for this k-map are equivalent.  
**a) True**                      b) False

**Problem 3 (11 pts): Design of Adders**

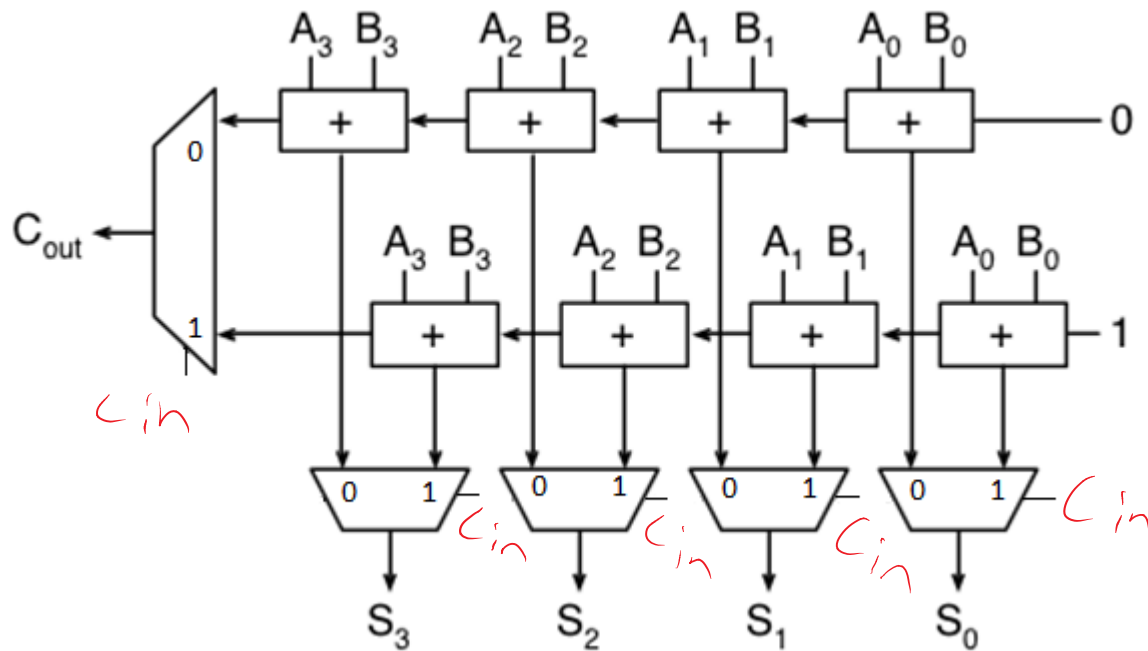
1. **(5 pts)** The circuit below implements a 4-bit, bit-sliced adder. It is composed of eight full adders and five multiplexers. Like the full adders we have seen before, this circuit can be combined in adder arrays to perform n-bit addition. Complete the design of the circuit by adding selection inputs to the MUXes.  
(Note: This is a different way to implement adders than what you have seen in class.)



**2. (6 points)**


a) The circuit below implements the carry out  $C_{out}$  of a full adder (circle one): True / **False**

Justify your answer.

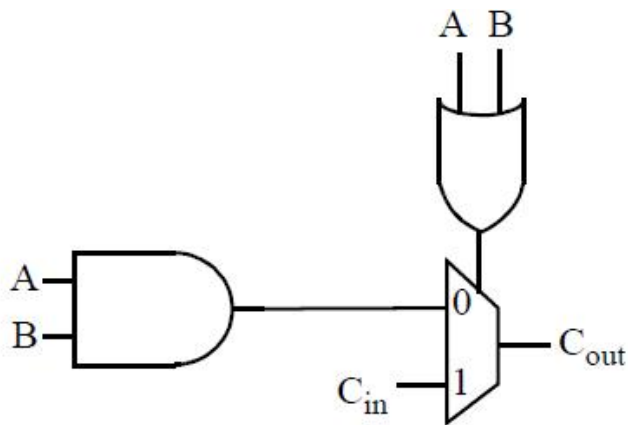


A	B	$C_{in}$	$C_{out}?$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

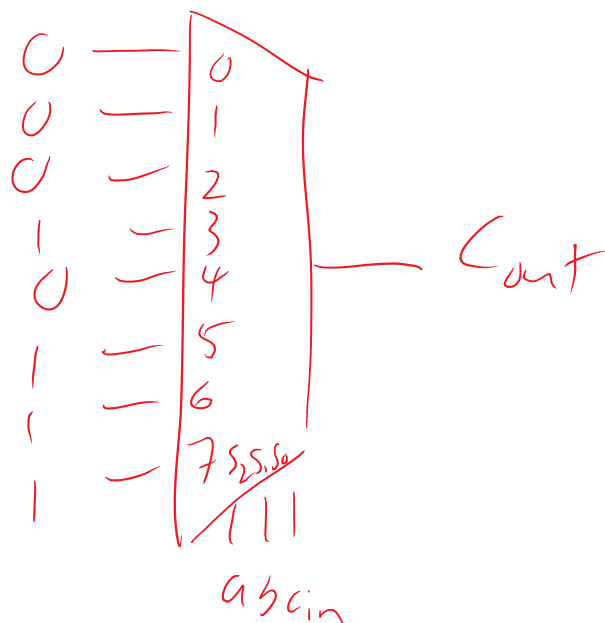b) If your answer to part a) was "False", implement the carry out of a full adder with a multiplexer. If your answer to part a) was "True", derive a different implementation of a carry out of a full adder with multiplexer



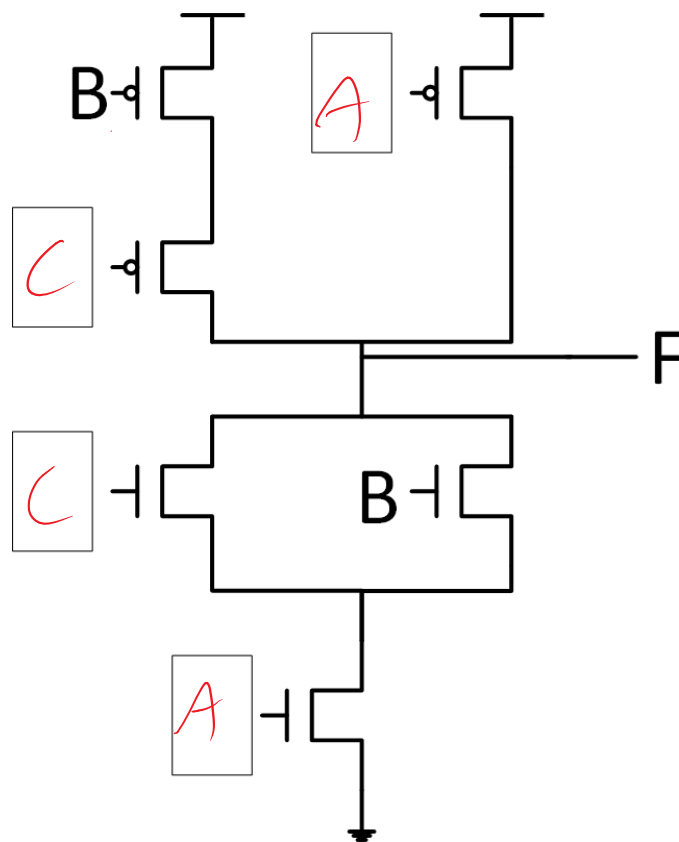**Problem 4 (9 pts): CMOS**


**(9 pts)** For the CMOS transistor circuit given in the figure below, complete the labeling of the circuit, as well as entries of the truth table that are not filled yet.



A	B	C	F
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

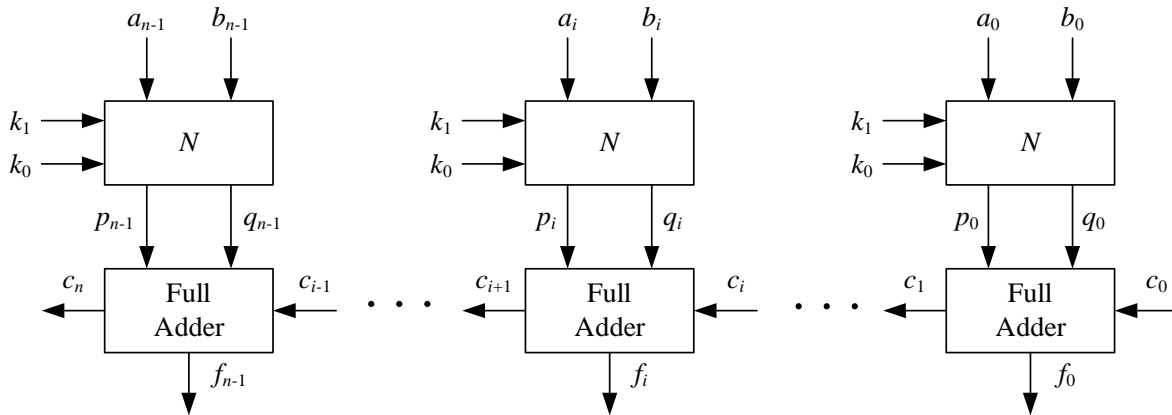**Problem 5 (17 pts): Arithmetic unit design**

Design circuit  $N$  such that the  $n$ -bit unit shown below performs the specified arithmetic operations for  $n$ -bit 2's complement inputs  $A = a_{n-1} \dots a_0$  and  $B = b_{n-1} \dots b_0$ :



1. (9 pts) Complete the table below to show how the outputs of circuit  $N$  relate to its inputs. Use only one of the values  $a_i$ ,  $b_i$ ,  $\bar{a}_i$ ,  $\bar{b}_i$ , 0, and 1 in each cell. One row has been completed for you.

Control Inputs		Operation	Full Adder Array Inputs		
$k_1$	$k_0$		$p_i$	$q_i$	$c_0$
0	0	$2 \cdot A$ (2 TIMES A)	$a_i$	$a_i$	0
0	1	$A - B$ (A MINUS B)	$a_i$	$\bar{b}_i$	1
1	0	A (PASS A)	$a_i$	0	0
1	1	$-B - 1$ (NEG B MINUS 1)	0	$\bar{b}_i$	0

2. (8 pts) Draw K-maps for outputs  $p_i q_i$  from circuit  $N$ . Each cell should have a 0 or 1.

$a_i b_i$


		00	01	11	10
00		0	0	1	1
01		0	0	1	1
11		0	0	0	0
10		0	0	1	1
$k_1 k_0$		$p_i$			

$a_i b_i$

		00	01	11	10
00		0	0	1	1
01		1	0	0	1
11		1	0	0	1
10		0	0	0	0
$k_1 k_0$		$q_i$			

**Problem 6 (17 pts): Flip flops, latches, and timing diagrams**

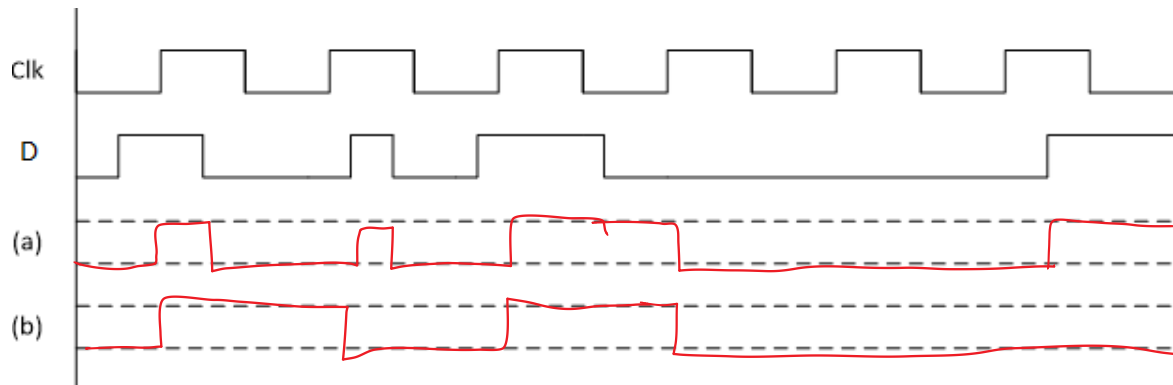1. (6 pts) Given timing diagram below, indicate the output of a D latch/flip flop assuming
- It is a clocked, gated, level sensitive latch
  - It is a positive edge triggered flip flop




2. (3 pts) You have seen a JK flip flop in your discussion. The characteristic equation (expression) for  $Q^+$  of a JK flip flop is given below:

$$Q^+ = QK' + Q'J$$

- a) Write the characteristic equation (expression) for  $Q^+$  of a **D flip flop**.

$$Q^+ = D$$

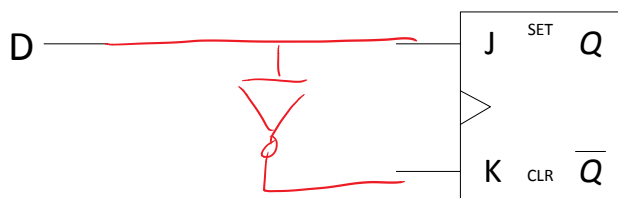- b) In the figure below, implement the functionality of a D-flip flop using a JK flip flop. Comparing the characteristic equations of a D and JK flip-flop may be helpful.





**3. (8 pts)** Consider a 3-bit shift register that has the functionality specified in the table to the right. Answer the following questions about the behavior and implementation of the shift register.


$F_1$	$F_0$	Operation
0	0	Circular shift right
0	1	Logical shift right
1	0	Arithmetic shift right
1	1	Unused

a) The shift register initially stores 110, what is stored in the register after one clock pulse and

$F_1F_0 = 00$ ? 011

$F_1F_0 = 10$ ? 111 (Assume again that 110 is stored before the operation)

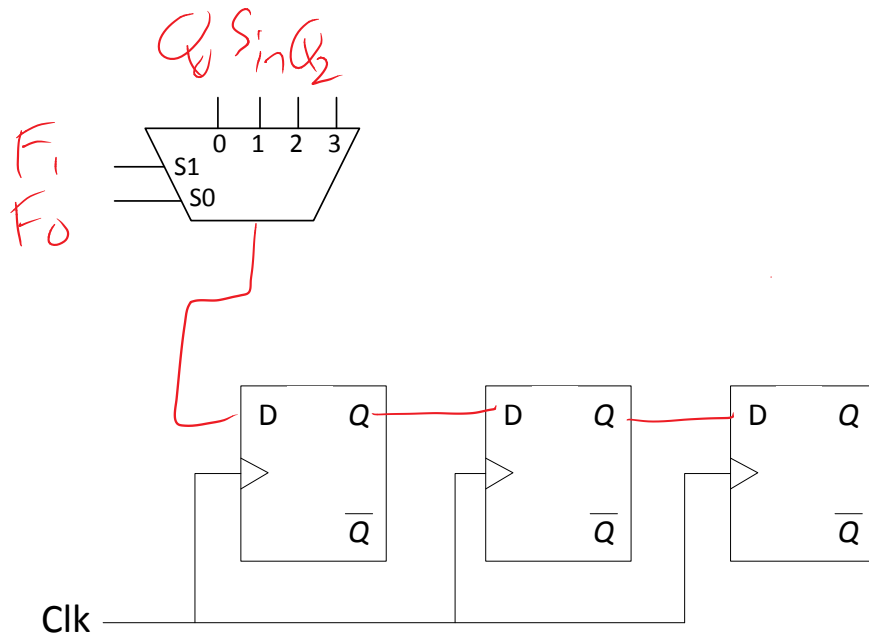b) Complete the design of a 3-bit register that performs the operations listed in the table. Serial input is labeled as  $S_{in}$ .



**Problem 7 (12 pts): Combinational logic design**

Design a 2-bit comparator circuit that compares two 2-bit unsigned binary numbers  $A = a_1a_0$  and  $B = b_1b_0$ . The circuit should output 1 if and only if  $A \geq B$ .


1. (4 pts) Use the kmap below, to specify how your quality control circuit should be built

		$b_1b_0$			
		00	01	11	10
$a_1a_0$	00	1	0	0	0
	01	1	1	0	0
	11	0	1	1	1
	10	0	1	0	1


2. (2 pts) Derive a minimal SOP expression from your kmap.

$$f(a,b,c_{in},c_{out}) = \underline{b_1b_0 + a_0\bar{b}_1 + a_1\bar{b}_1 + a_1a_0 + a_1\bar{b}_0}$$

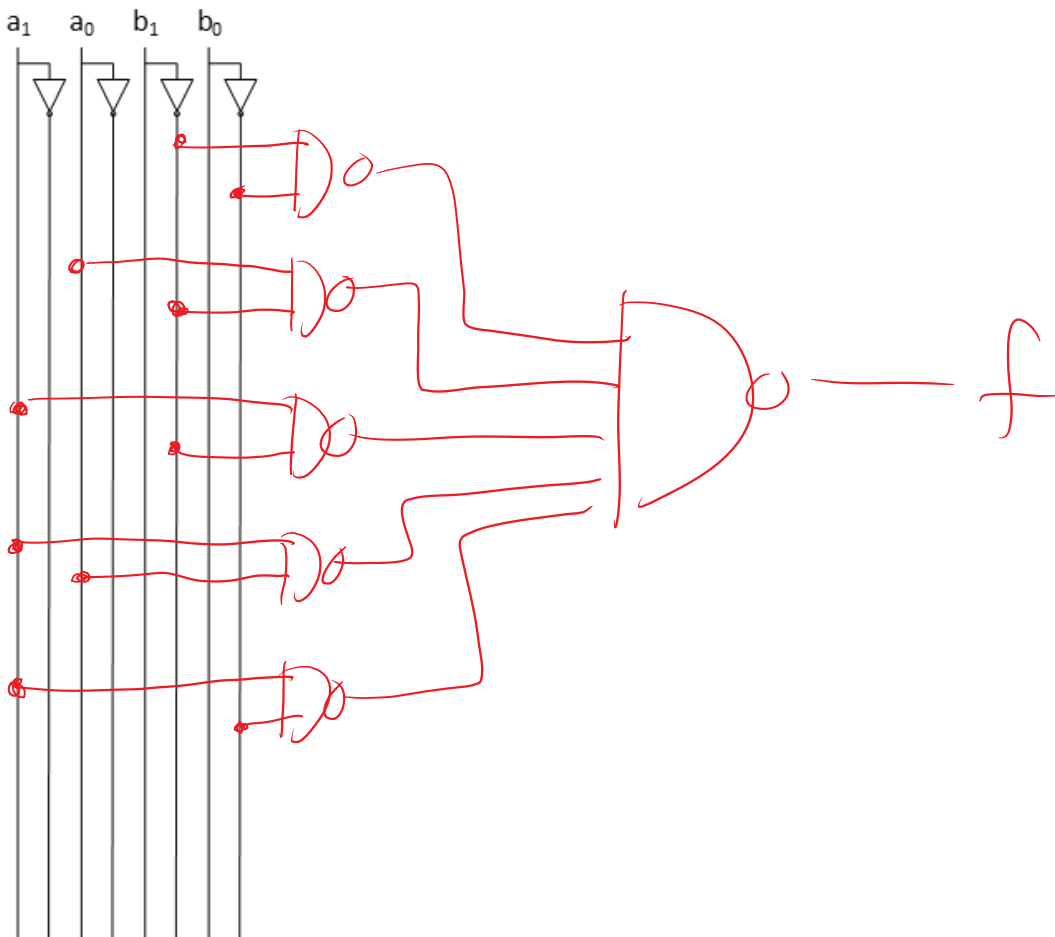3. (3 pts) Show a 2-level NAND only implementation of your circuit below.



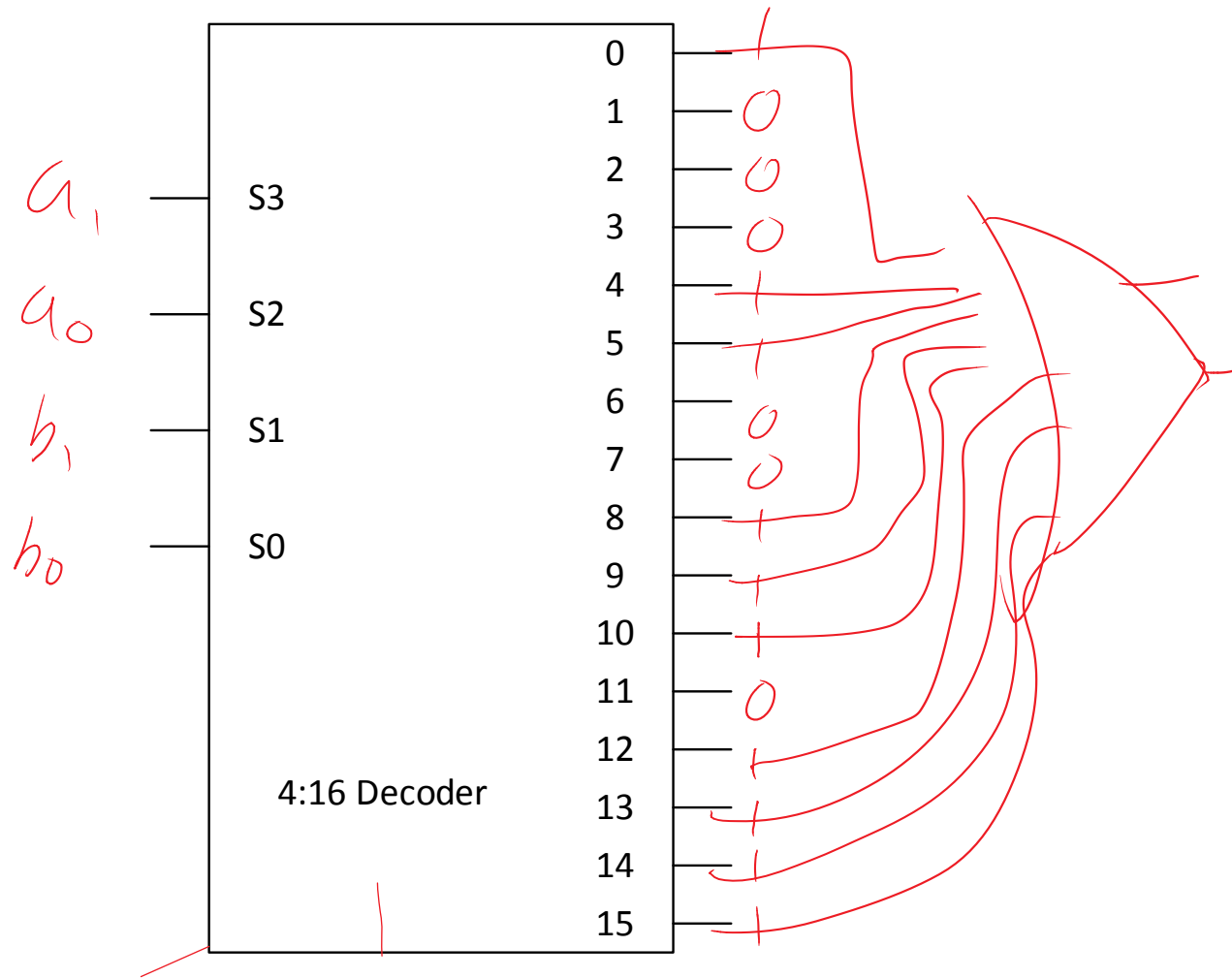4. **(3 pts)** Using the figure below, implement the 2-bit comparator circuit using a decoder and as few additional logic gates as possible.



**Problem 8 (10 pts): Boolean algebra in C**

1. (8 pts) Implement a program in C that prints canonical POS representation for function  $g(a,b,c) = (ab + \bar{b}c)$  using Maxterm notation. The program is partially implemented, you only need to complete some parts of it. **Use bit-wise and arithmetic operators only.**

```
#include <stdio.h>

int main()
{
    unsigned int a,b,c;
    int g;
    int i;
    int first=1;

    for ( a=0; a <= 1; a++ )
    {
        for ( b = 0; b <= 1; b++ )
        {
            for ( c = 0; c <= 1; c = c + 1 )
            {
                g = ~((a & b) | (~b) & c) & 1; /* function g */
                if (g == 0)
                {
                    i = 4*a + 2*b + c; /* maxterm index */
                    if(first){
                        printf("g(a,b,c)=M%d", i);
                        first = 0;
                    }
                    else printf("M%d", i);
                }
            }
        }
    }

    printf("\n");

    return 0;
}
```

2. (2 pts) Write down EXACTLY the formatted text that will be printed on the terminal screen by the program.

$$g(a,b,c) = m_1 m_5 m_6 m_7$$

**Boolean algebra properties**

Commutativity	$x \cdot y = y \cdot x$	$x + y = y + x$
Associativity	$(x \cdot y) \cdot z = x \cdot (y \cdot z)$	$(x + y) + z = x + (y + z)$
Distributivity	$x \cdot (y + z) = x \cdot y + x \cdot z$	$x + y \cdot z = (x + y) \cdot (x + z)$
Idempotence	$x \cdot x = x$	$x + x = x$
Identity	$x \cdot 1 = x$	$x + 0 = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$
Complementarity	$x \cdot x' = 0$	$x + x' = 1$
Involution		$(x')' = x$
DeMorgan's	$(x \cdot y)' = x' + y'$	$(x + y)' = x' \cdot y'$
Absorption	$x \cdot (x + y) = x$	$x + x \cdot y = x$
No-Name	$x \cdot (x' + y) = x \cdot y$	$x + x' \cdot y = x + y$
Consensus	$(x+y) \cdot (y+z) \cdot (x'+z) =$ $(x+y) \cdot (x'+z)$	$x \cdot y + y \cdot z + x' \cdot z =$ $x \cdot y + x' \cdot z$